


All the memory chips rely on the concept of time introduced into the circuit. Which makes these chips “sequential” instead of “combinational”.

Sequential chips will use a **clock** as an input. From a logic perspective, the clock is assumed **built-in** (it depends on the physics of semiconductors: resistors, capacitors, oscillators..., it will be considered out of the scope for “Elements of Computing System”)


In the book, the D flip flop is also considered **built-in**, (due to the limitation in the HDL of not being capable of recursiveness--mapping the output of one chip into other chips that serve as inputs again, that is, a feedback loop).

However, to understand better how the flip flop gets created, it’s good to see the videos “SR latch” and then “D flip flop” in the references.




## SR LATCH

 

=>

 


=>

   


from these "balanced" states, the only remaining option is when both S and R are turn to 1, in this case the chip just returns the same previous state.

atch

 

S	R	Q	$\bar{Q}$	Comments
0	0	NC	NC	No Change (remain present state)
0	1	0	1	RESET
1	0	1	0	SET
1	1	0	0	INVALID

Data flip flop:

 

Q	D	Q(t+1)
0	0	0
0	1	1
1	0	0
1	1	1

To remember:

- Latches serve to store a bit-state. That's the "No Change" value in their truth tables.
- When a latch is regulated by a clock input, it becomes a **flip-flop**.